




Electricity



ELECTRICITY comes from the **electrons** in an atom.

Electrons

Negative Charge

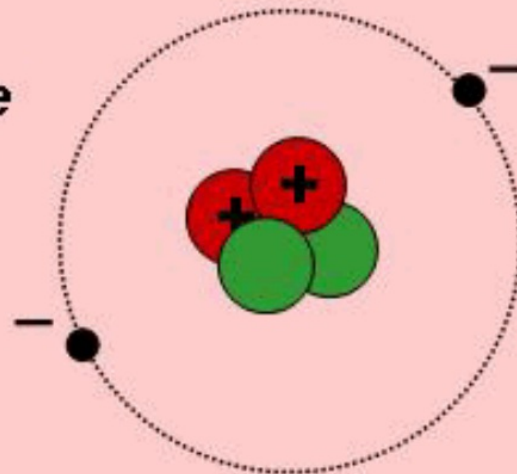

Electricity

Forms when **electrons are transferred**
between objects.



Types of Electricity



Static Electricity

- Build-up of electrical charge
- Electrons move in non-specific directions

Current Electricity

- Flow of electricity through wires
- Electrons move in definite paths





Electricity exists naturally in nature...

Static Electricity


For example:

Lightning

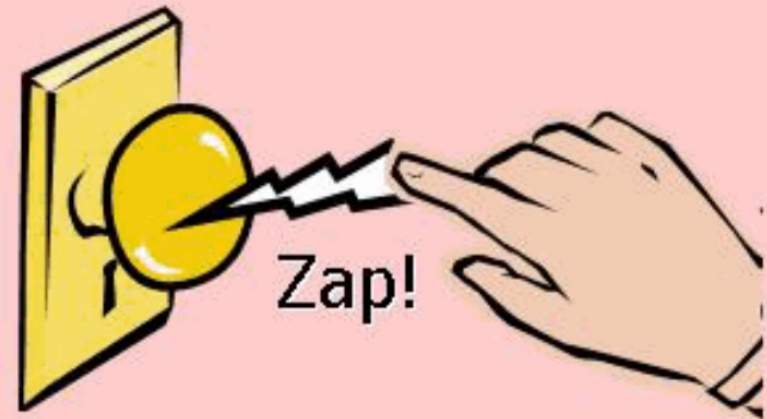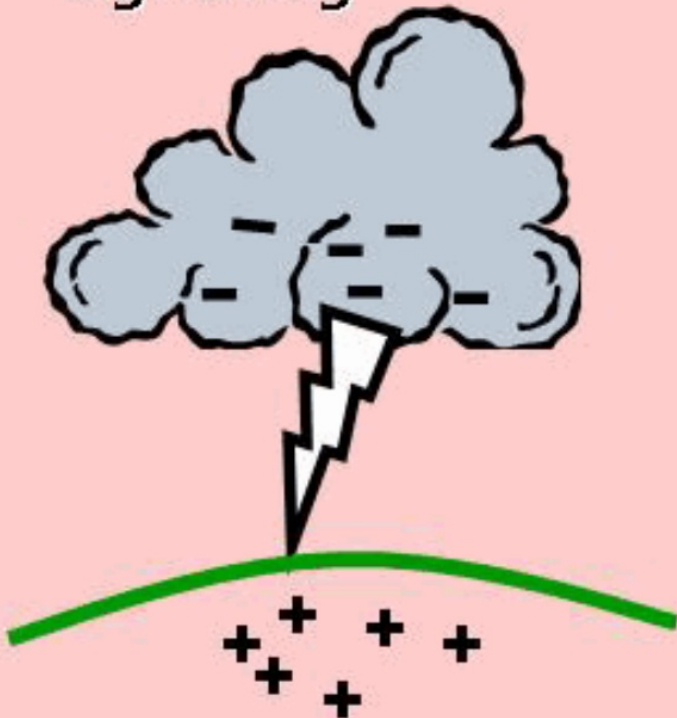

Law of Electrical Charges


Opposite Charges Attract

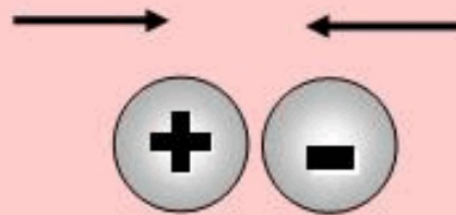

Same Charges Repel



Battery

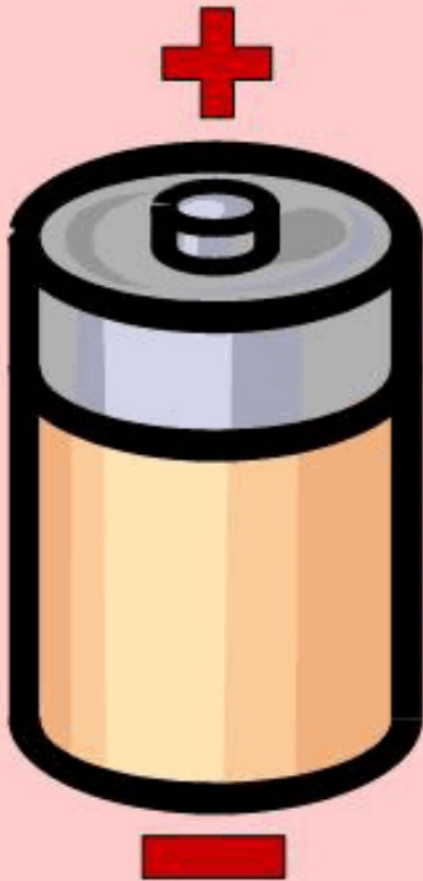

Batteries use chemical energy to move electrical charges


Types:

Dry cell-chemical inside are a paste and do not spill easily (example: AA or AAA batteries)


Wet cell-chemicals inside are free flowing and could spill if turned upside down (example: car battery)

Electric current in a circuit

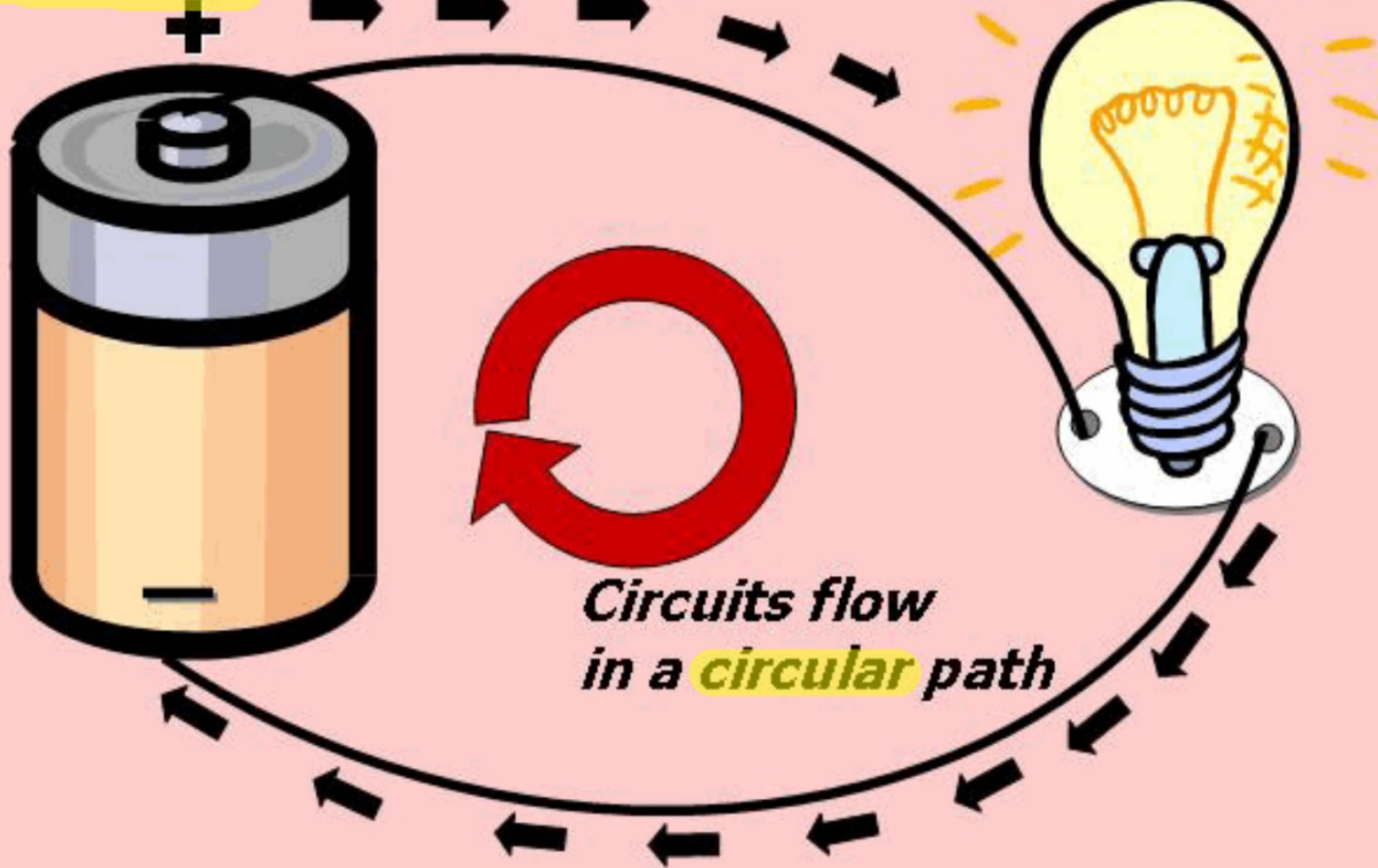Electric current flows from
positive (+) to negative (-)




Open Circuit

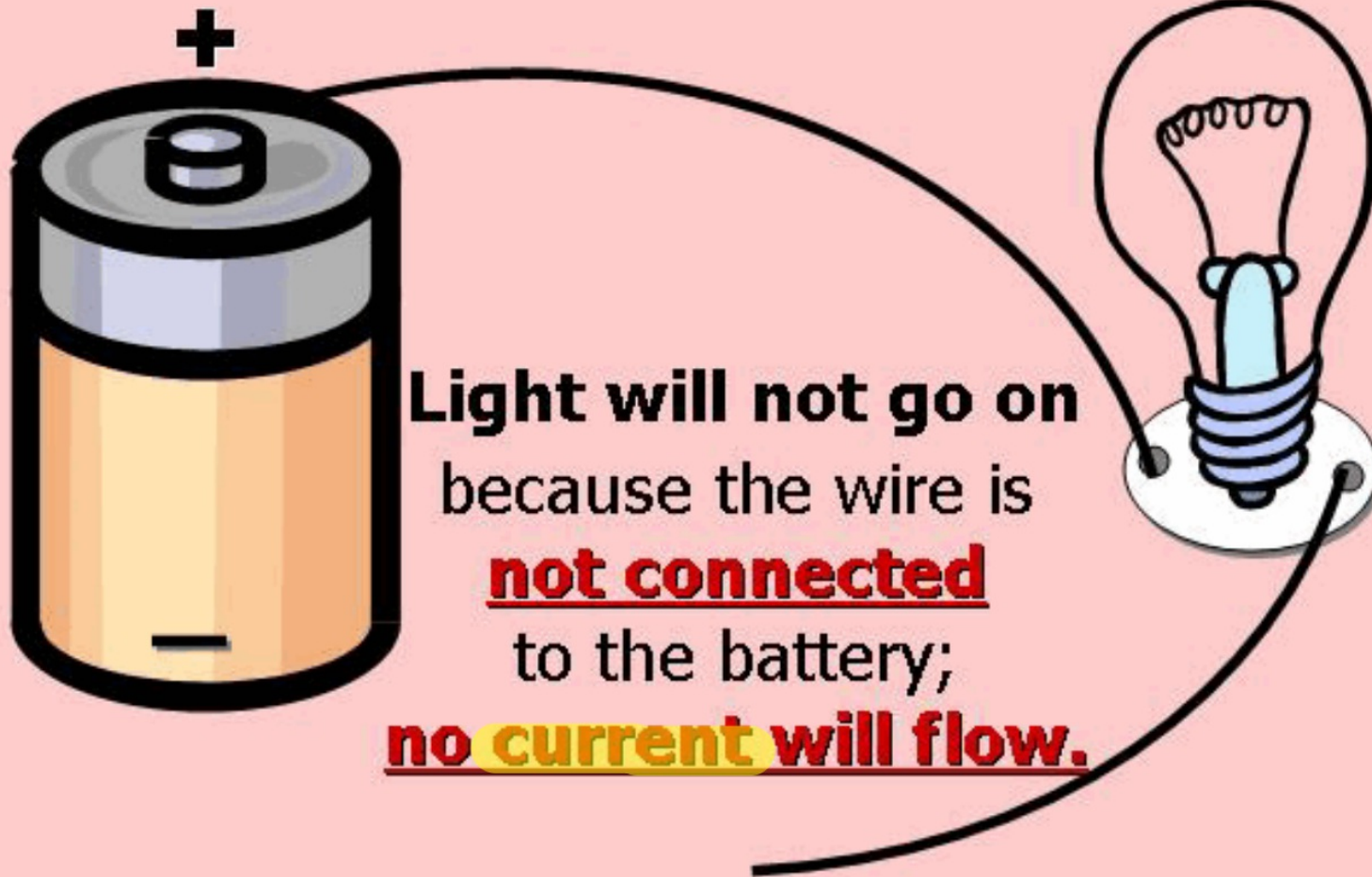

Light will not go on
because the wire is
not connected
to the battery;
no current will flow.


Closed Circuit

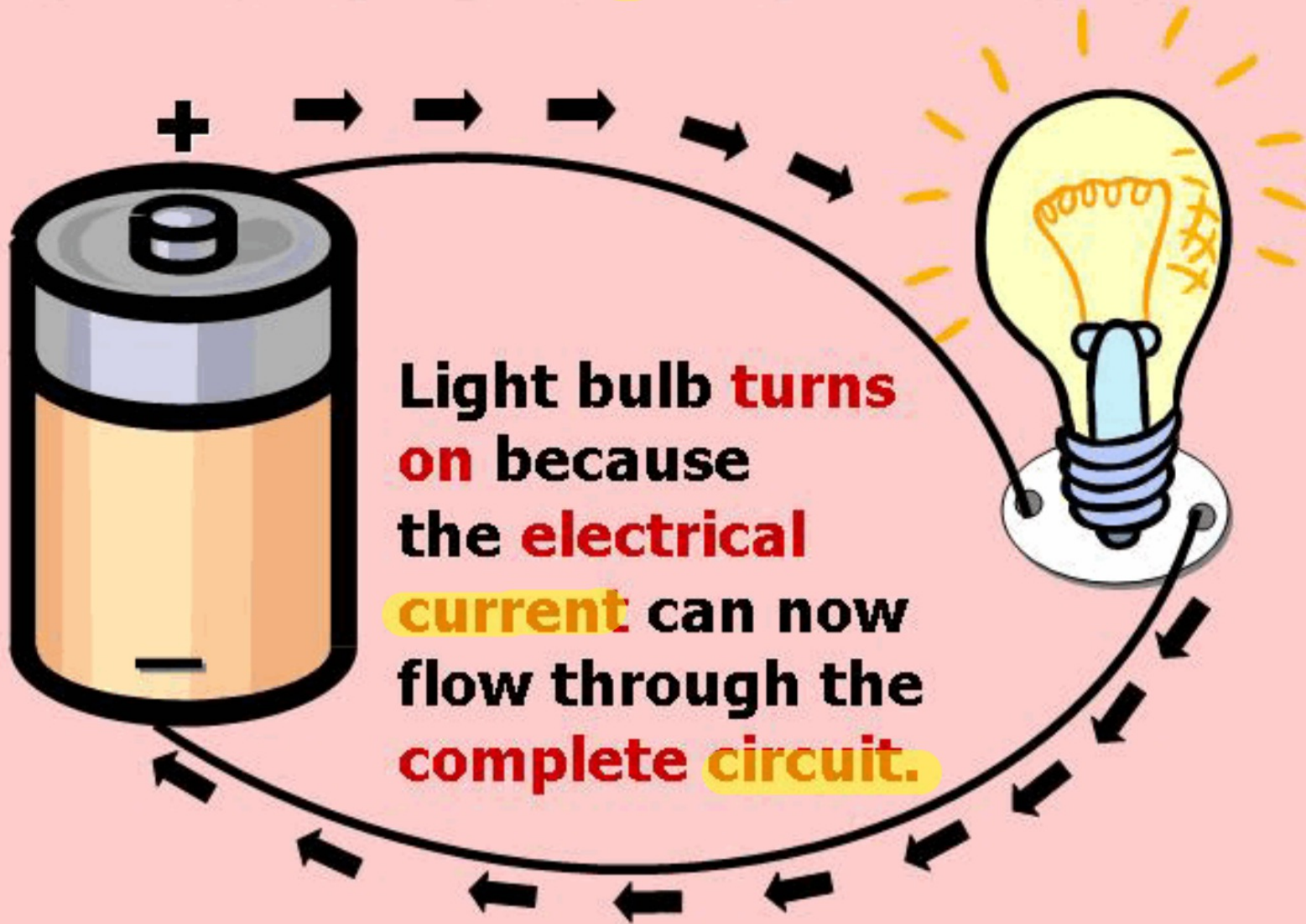

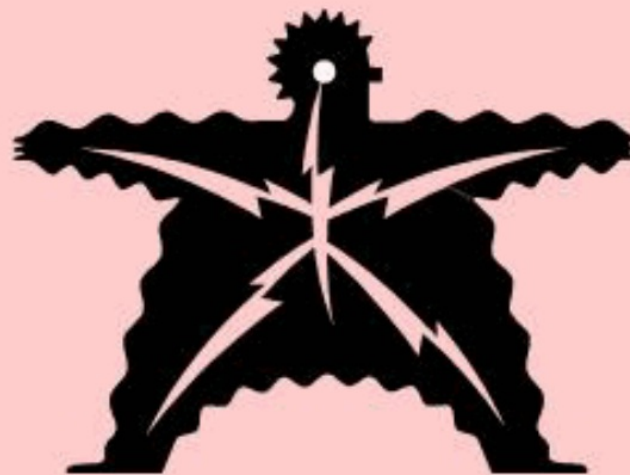Light bulb **turns on** because the **electrical current** can now flow through the **complete circuit.**











Short Circuits


- an **accidental** path for current to flow
- often causing risk of **shock** or **fire**
- a branch with zero or **very low** resistance




(MORE ON NEXT SLIDE)

Circuit Diagrams

- Wire 
- Power Source (1.5 V) 

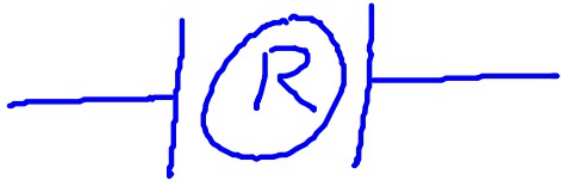- Bulb 

- Resistance 

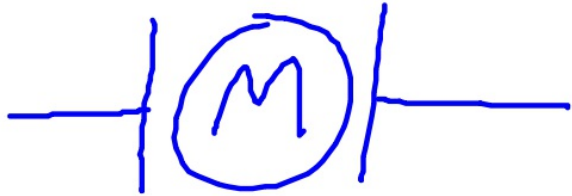- Switch 

open 
closed



Variable Resistor
ex: Dimmer Switch



Motor




Capacitor
ex: Flash on a disposable camera

Energy Conversions in a Simple Circuit

**Battery converts
Chemical Energy
into...**


Electrical Energy

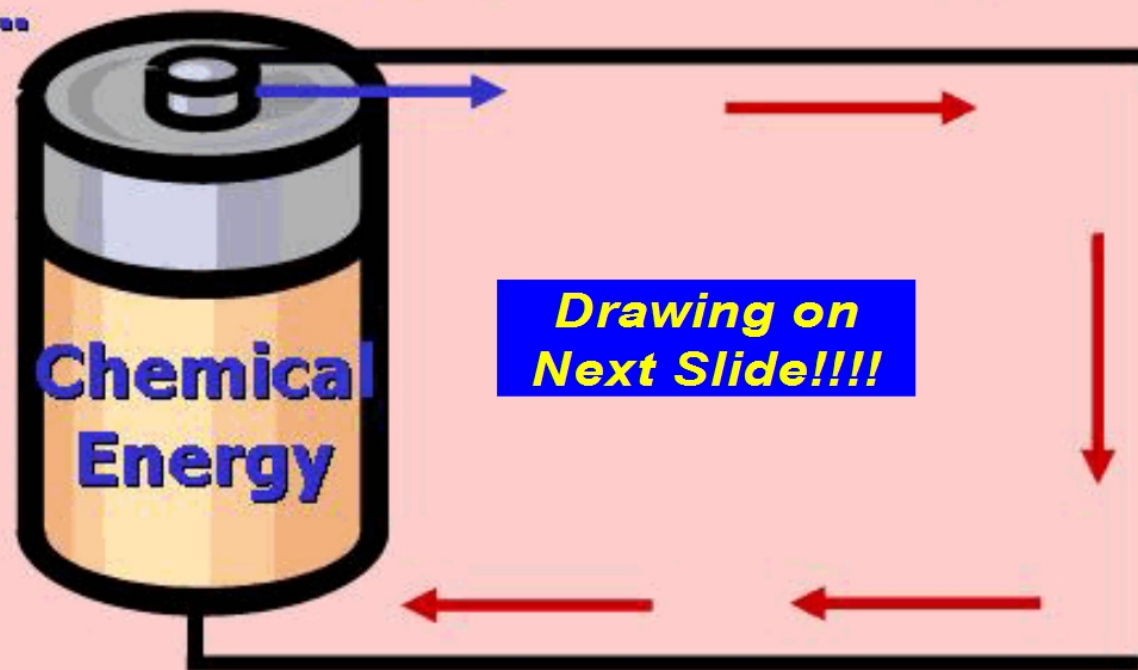

**If you add a light
bulb in the circuit,
electrical energy is
converted into...**




**Light Energy
and Thermal
Energy**

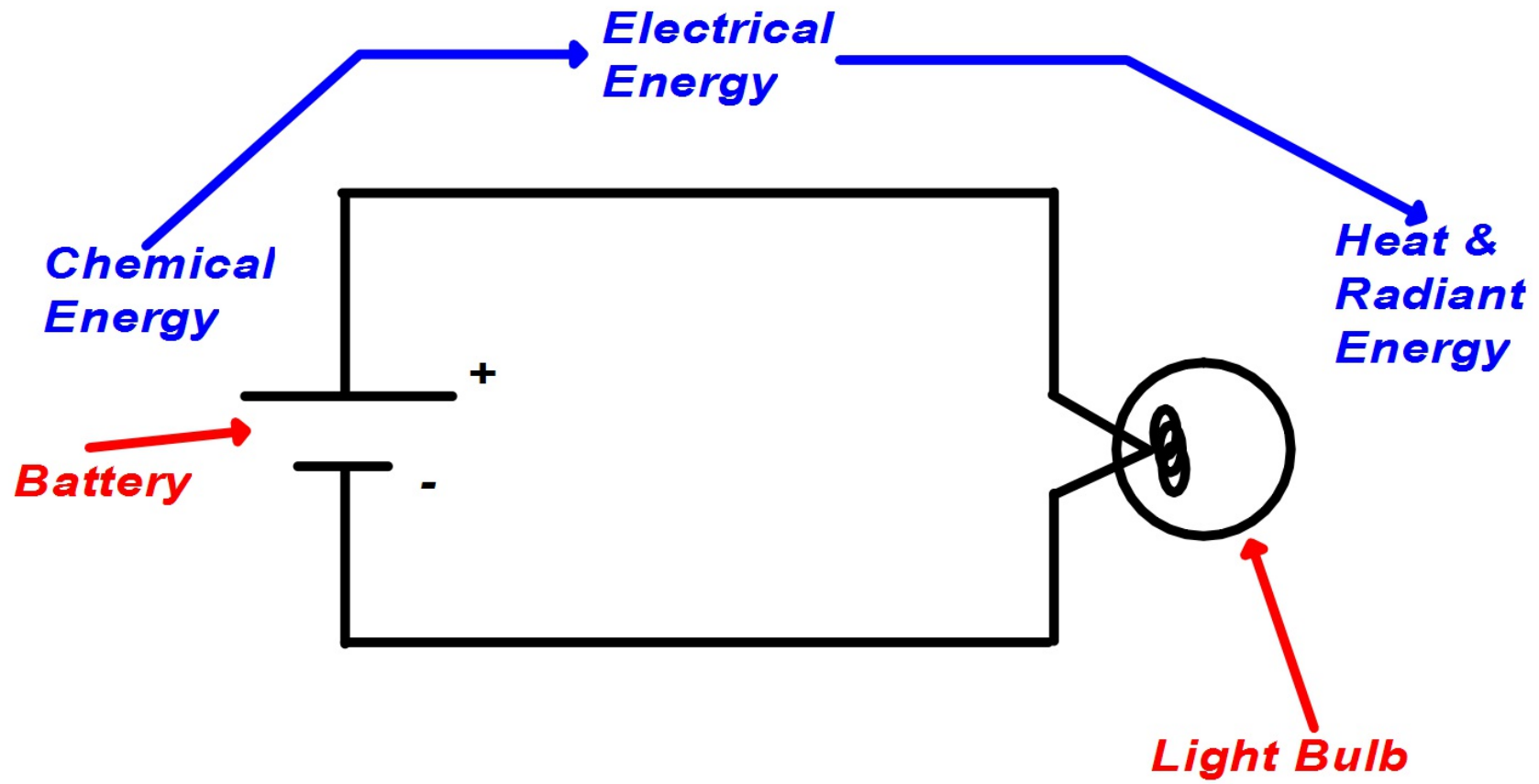

Volts

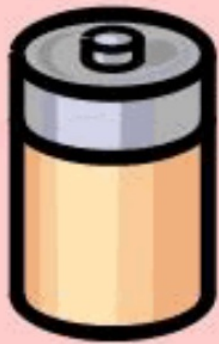Measurement of the **potential energy difference**




IF = 1.5 volts



1.5V



3.0V

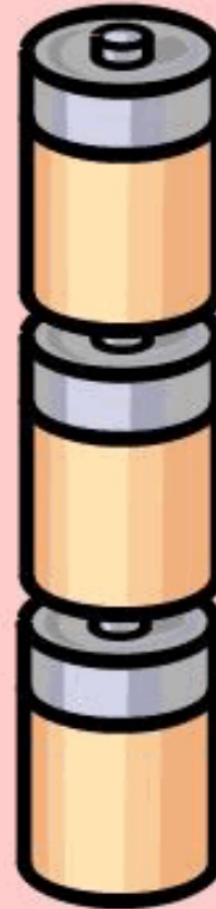


?V

Voltage

is a measure of "potential difference."

The unit for voltage is volts (V)

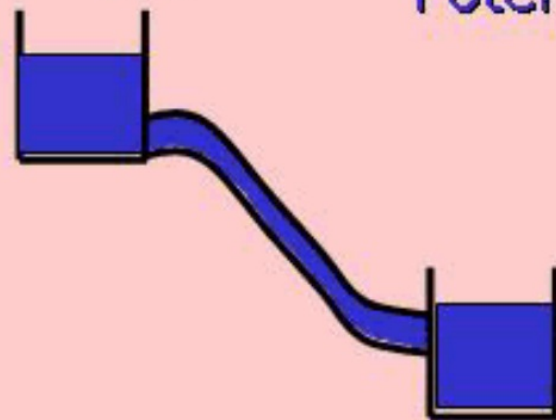from **Higher Energy**
Potential Energy
(height)




Potential Difference

1.5 Meters

To **Lower Energy**

1.5 V

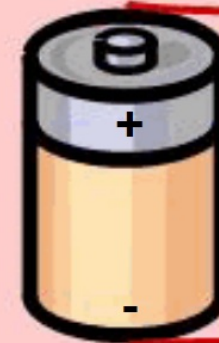


0.0 V

The **potential difference**
(voltage) is 1.5 V.

Voltage

The higher the energy, the greater the **voltage** (potential difference).

Higher Potential energy (height)

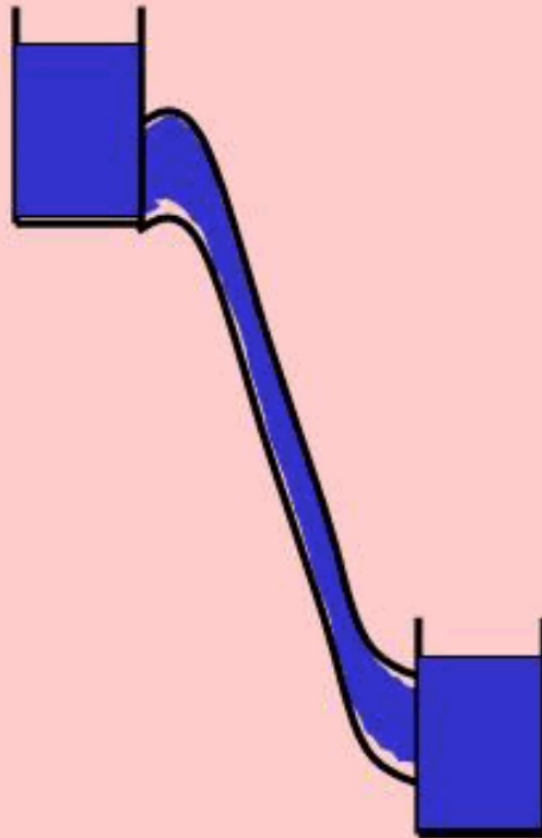

Greater Potential Difference

3.0 Meters

To Lower Energy


3.0 V



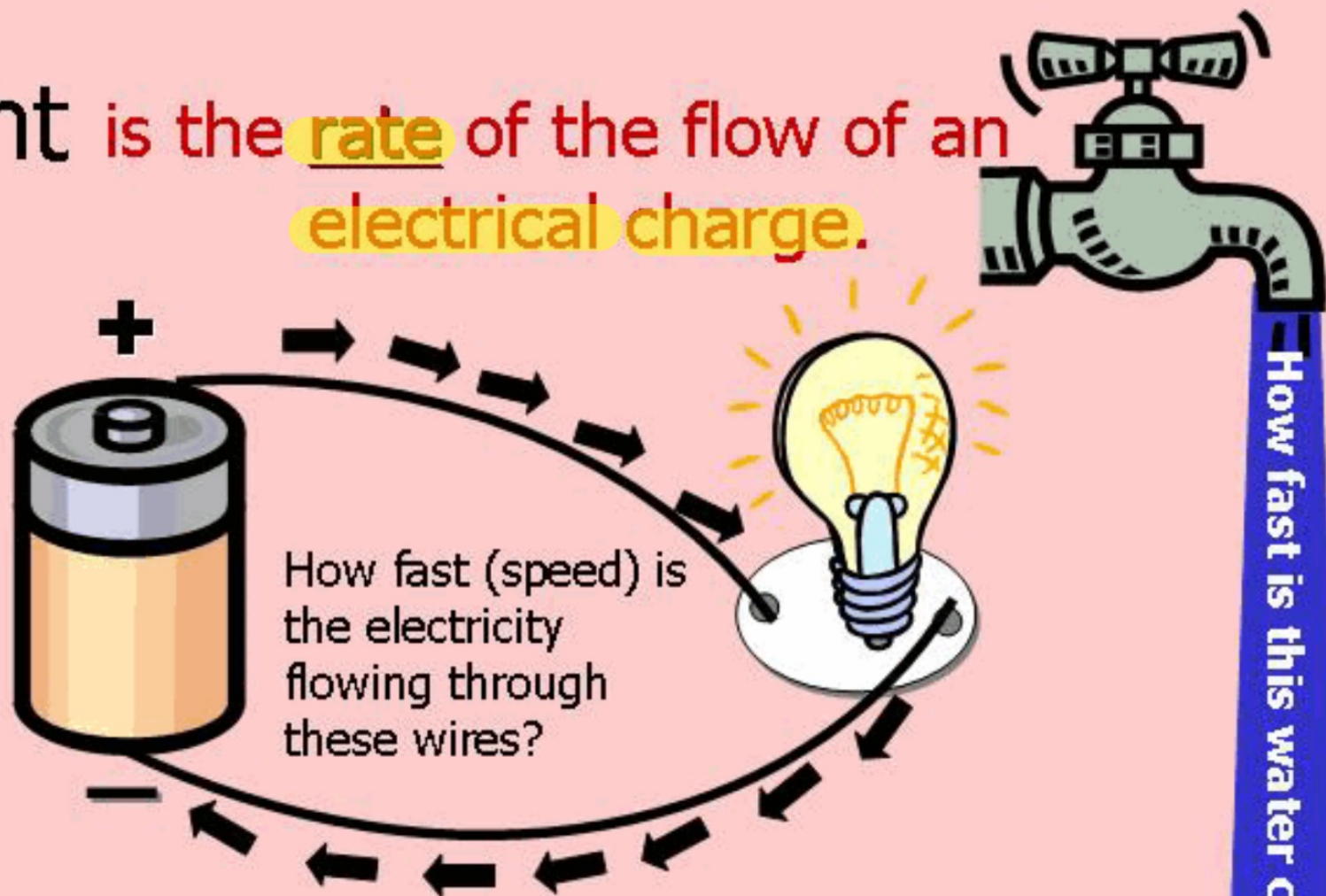0.0 V

The **potential difference** (voltage) is 3.0 V.

Current is the **rate** of the flow of an **electrical charge**.




The **rate** that the electricity flows is called **CURRENT**
CURRENT (I) is measured in **Amperes (Amps)**.

TYPES of CURRENT



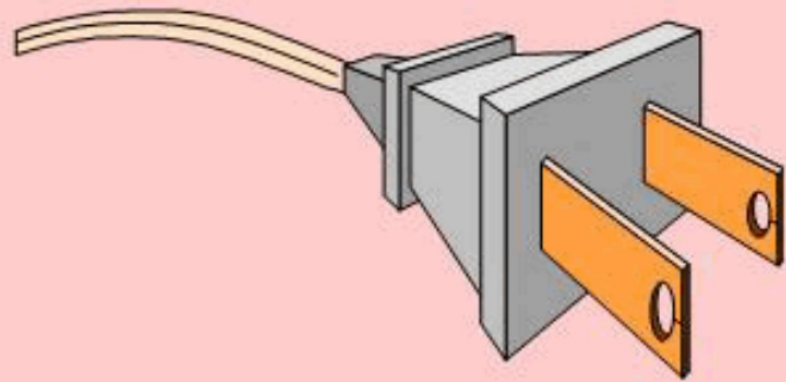Direct Current (DC)
flows in one direction.




Alternating Current (AC)
flows back and forth.

RESISTANCE

*the tendency of a material to **oppose** electron flow*

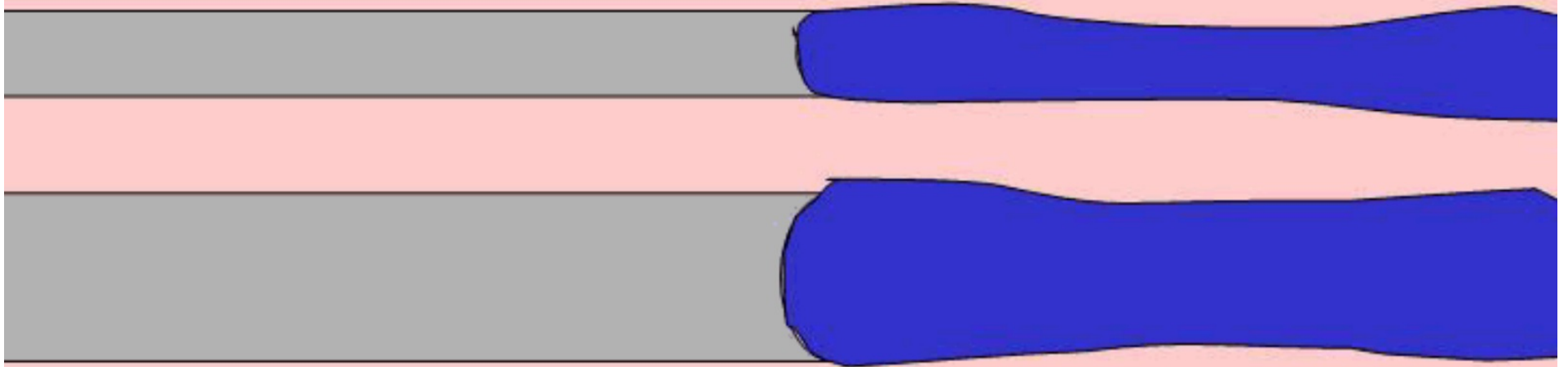Which of the pipes below would allow water out faster?



The smaller pipe would have more resistance to the flow.



Resistance (R) is measured in ohms.

Ω



to Electrical Current

Which of the following do you think would be most resistant to electrical current?



Plastic



Glass



Rubber



These materials **allow** electrical charge (current) to move easily through them. They have **little resistance** to the flow of electrical current. They are

Conductors.



Glass



Plastic



Rubber

These materials **do not allow** electrical charges (current) to move easily through them. They have a **strong resistance** to the flow of electrical current.

They are

Insulators.

Conductors and Insulators:

- Conductors allow charges to flow easily.
 - Examples include **copper**, **silver**, and **aluminum**.



- Insulators do not allow charges to flow easily
 - Examples include **glass**, **plastic**, and **rubber**

Rubber insulation →

