

# Semiconductors


- material that falls **between conductor** and **insulator** in terms of electrical conductivity
- computer chip (silicon), LED's, some lasers

# Wires carry an electrical charge.



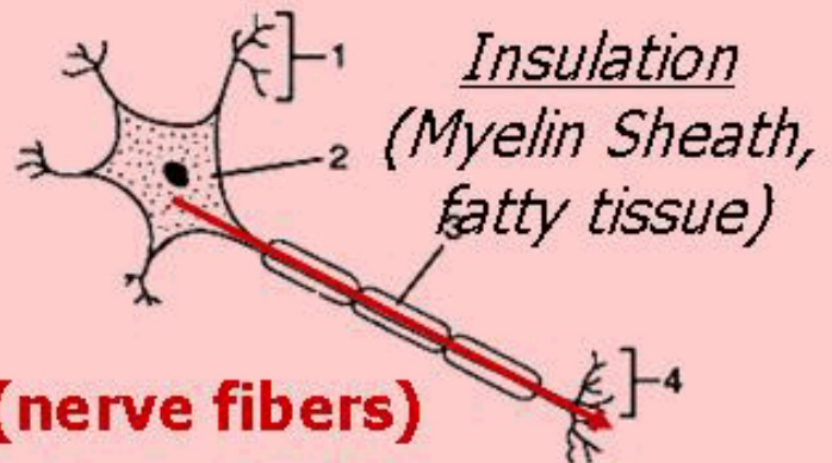**Copper wire covered in rubber insulation**

**The "human" wiring system:  
The neuron (nerve cell)**



**Wires (nerve fibers)**

Match the word on the left to the phrase on the right.

**Resistance**

(R) in Ohms  $\Omega$

**Current**

(I) in Amps

**Voltage**

(V) in Volts

How Fast?

How much?

How much is it slowed down?

# Household Current

## Alternating current

- direction of the current goes back and forth, 60 times per second,
- example wall socket, 120 volts

## Direct current

- current flows in one direction
- batteries only-AAA, AA, C, D cell batteries all are 1.5 volts each, the difference in size means it should last longer

# Safety devices

**fuse**-small piece of metal that melts if the current becomes too high opening switch


**circuit breaker**-piece of metal that bends when it gets over heated opening switch because current is too high

**GFI-ground fault interrupter**, usually found in bathrooms or garages shuts off plug when current is too high.

# Electrical Measuring Instruments

- Voltmeter-used in parallel to measure voltage
- Ammeter-used in series to measure current
- Galvanometer-use to detect a current
- Ohmmeter-measures resistance

Georg  
Simon  
Ohm

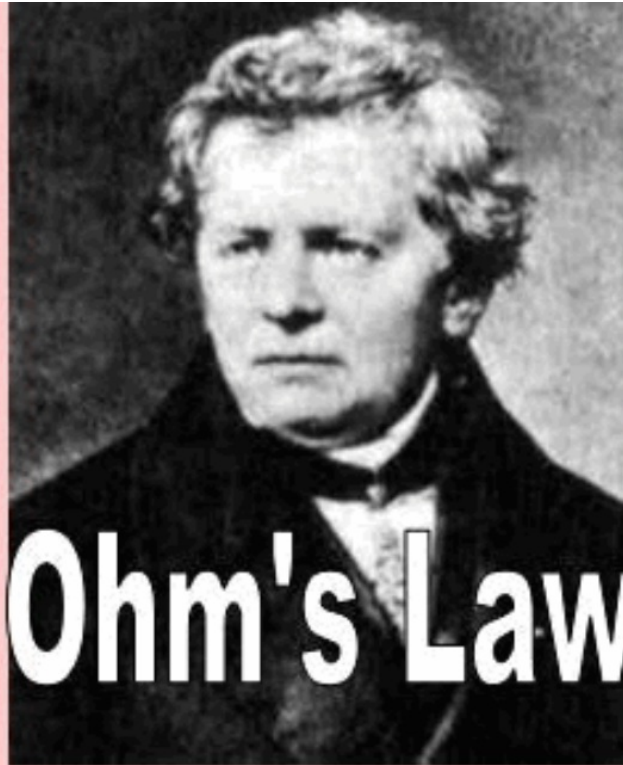

$$V = I \times R$$

**We can use this formula to figure out  
volts, current and resistance.**

# Ohm's Law Formula

$$V = I \cdot R$$

Symbol	Name	Unit	Unit Symbol
<b>V</b>	<b>Voltage</b>	<b>Volts</b>	<b>v</b>
<b>I</b>	<b>Current</b>	<b>Amps</b>	<b>A</b>
<b>R</b>	<b>Resistance</b>	<b>Ohms</b>	<b>Ω</b>



## Example: Ohm's Law Problem

Calculate the potential different (volts) across a  $3 \Omega$  resistor if a  $0.5 \text{ A}$  current is flowing through it.

g)  $R = 3 \Omega$   
 $I = 0.5 \text{ A}$

s)  $V = (0.5 \text{ A})(3 \Omega)$

u)  $V = ?$

e)  $V = I \cdot R$

s)  $V = 1.5 \text{ V}$

# Power Formula

Electrical Power = the rate at which energy flows

$$P = I \cdot V$$

Symbol	Name	Unit	Unit Symbol
<b>P</b>	<b>Power</b>	<b>Watts</b>	<b>w</b>
<b>I</b>	<b>Current</b>	<b>Amps</b>	<b>A</b>
<b>V</b>	<b>Voltage</b>	<b>Volts</b>	<b>v</b>

## Example: Electrical Power Problem

If a CD player uses 4.5 v with 0.2 amps of current, what is the Power it uses?

g)  $V = 4.5\text{v}$   
 $I = 0.2\text{A}$

s)  $P = (0.2\text{A})(4.5\text{v})$

u)  $P = ?$

e)  $P = I \cdot V$



s)  $P = 0.9\text{w}$

# TYPES OF CIRCUITS


Series Circuits- an electrical circuit with **only one path**

Parallel Circuit- an electrical circuit with **more than one path**

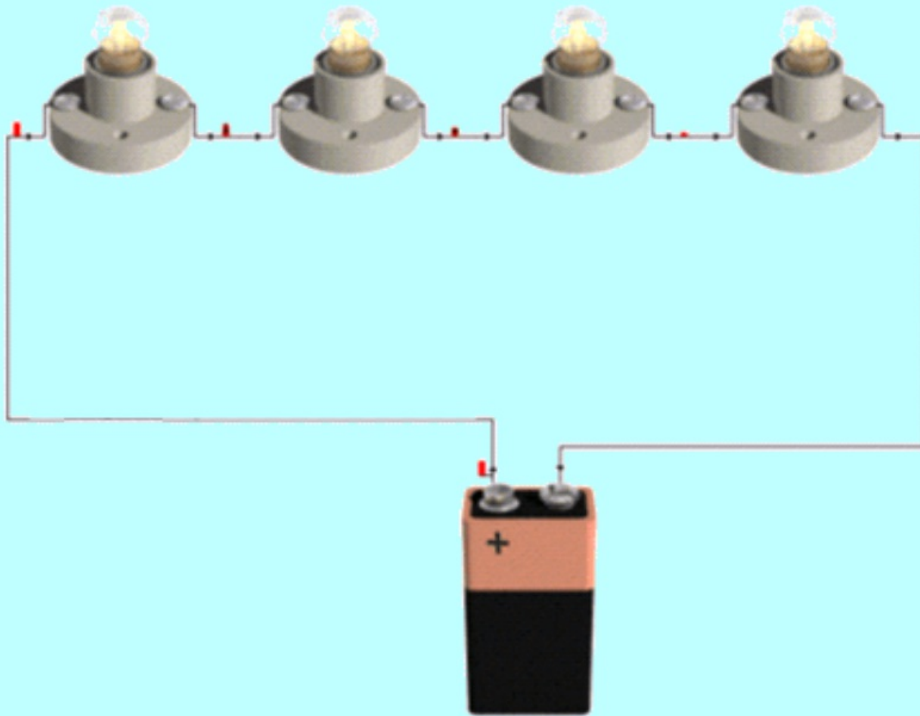
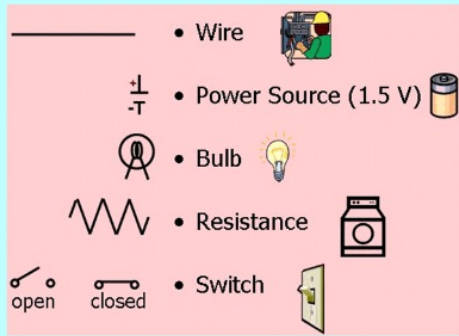
# Draw circuit diagrams and label these circuits as parallel or series.



What do you notice about the lights?

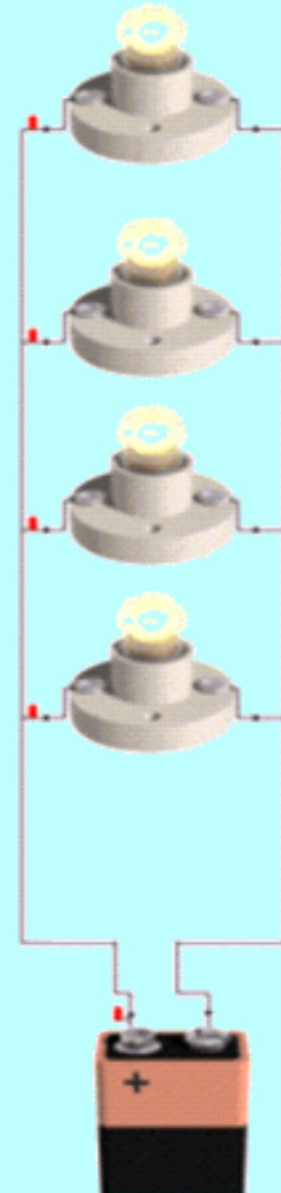


**What it should look like**

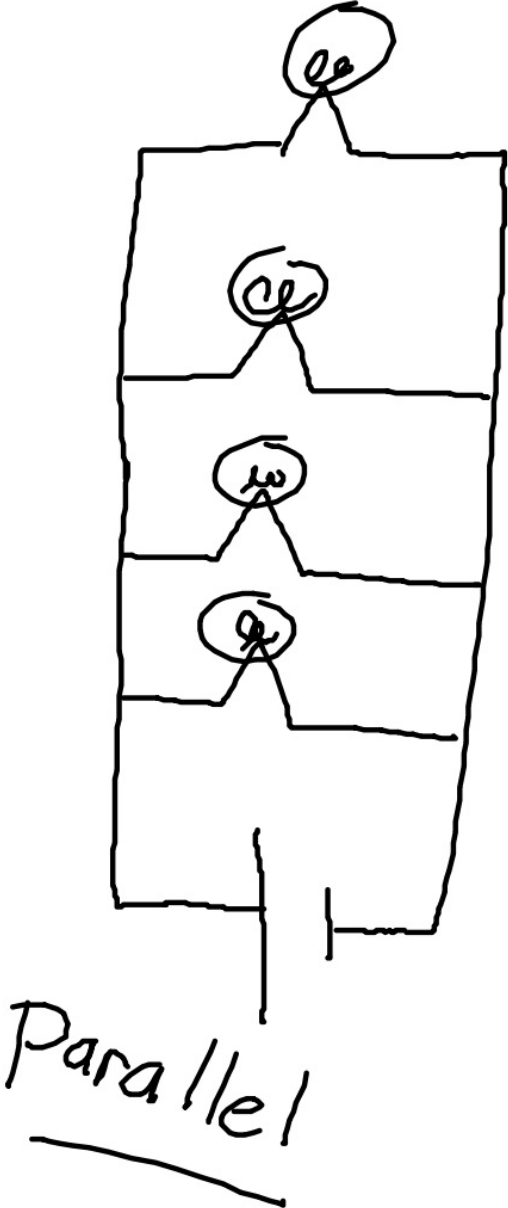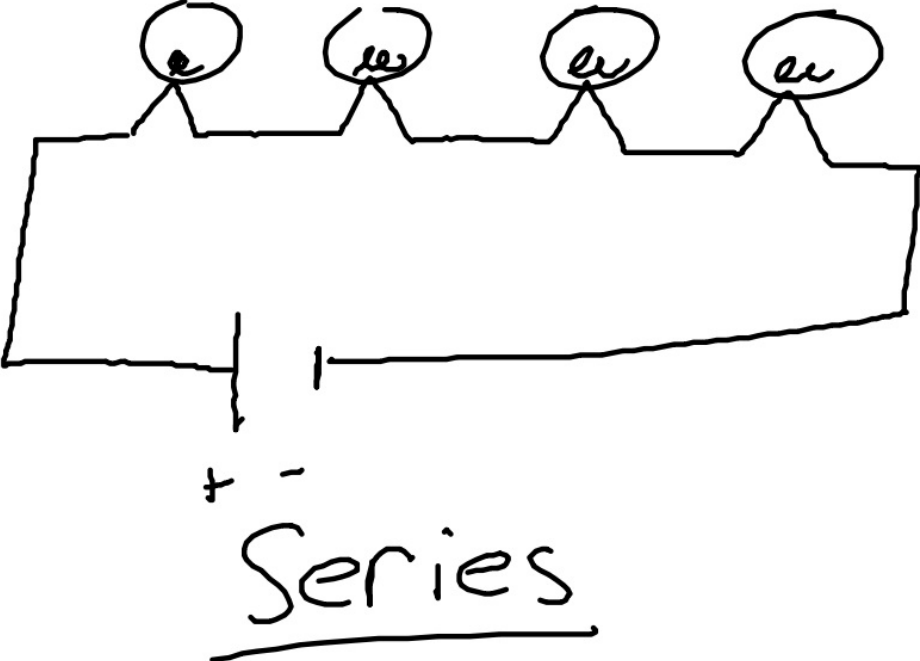

# Series Circuits



**The light bulbs turn on.**

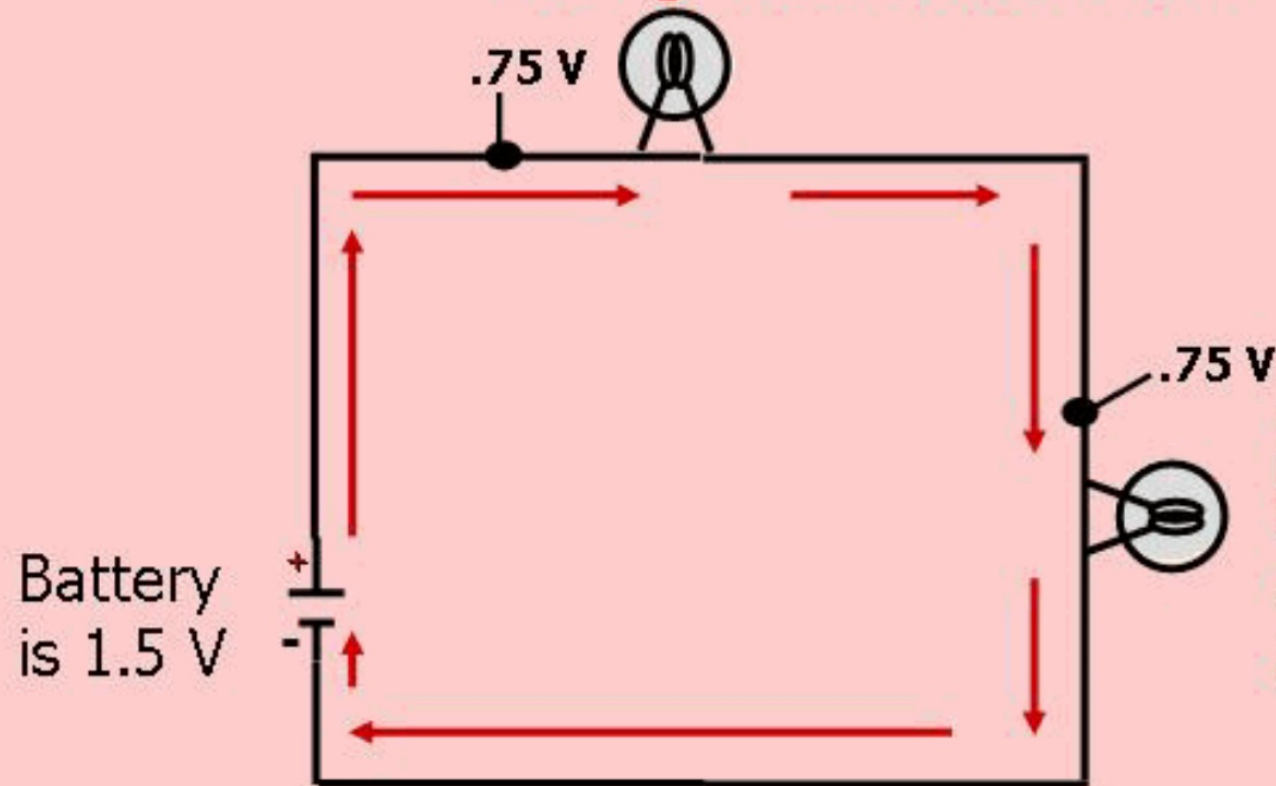

**However, since the voltage drops, the lights are dimmer.**

# Series Circuits

**If this light bulb does not turn on,**

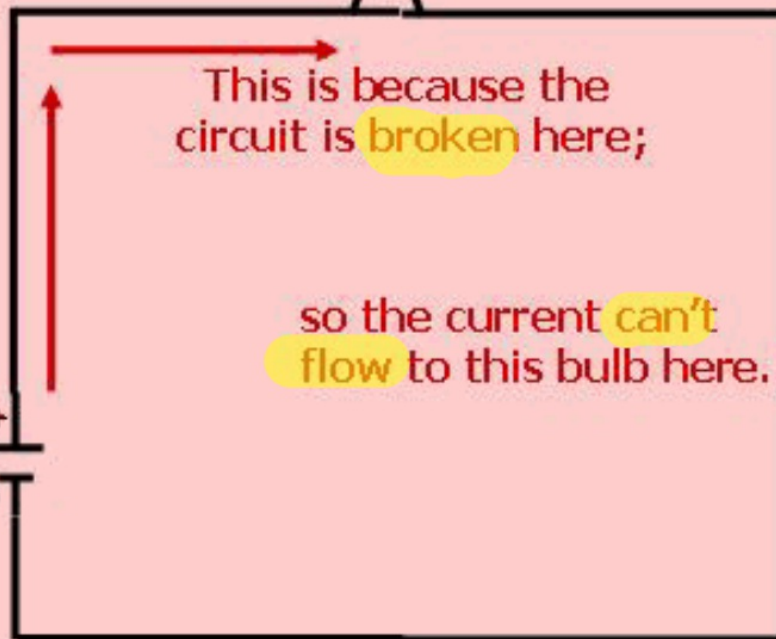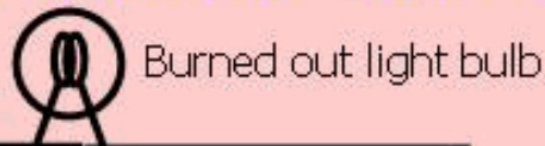

**neither light bulb will turn on.**



Christmas lights are commonly made this way.



# Series Circuits Info


- The current has **only one path** it can travel along
- One light goes out **all lights out**-open circuit
- Imagine if you turned off one light in your house that means that the circuit is broke and **everything** else goes off. Everything would have to be turned on to keep things running.
- Current is the **same** at all points
- Voltage is **reduced** by each **resistance** (light bulb, motor, heaters)
- **Voltage drop**-each separate resistor causes volts to drop

# Kirchhoff's Voltage Law

- The total of all voltage **drops** must add up to the total voltage **supplied** by the battery (energy in)
- $+1.5 \text{ V} - 0.5 \text{ V} - 0.5 \text{ V} - 0.5 \text{ V} = 0$   
battery    bulb    bulb    bulb


# Parallel Circuits

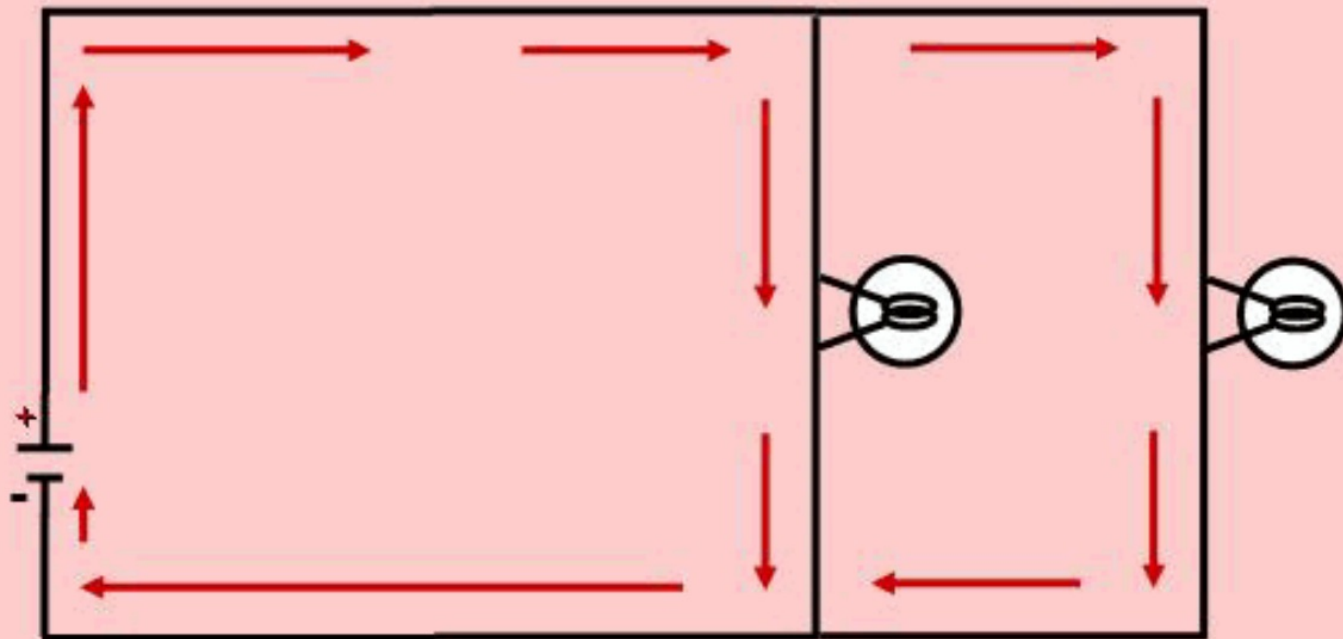**Current divides and has more than one path.**




# Parallel Circuits

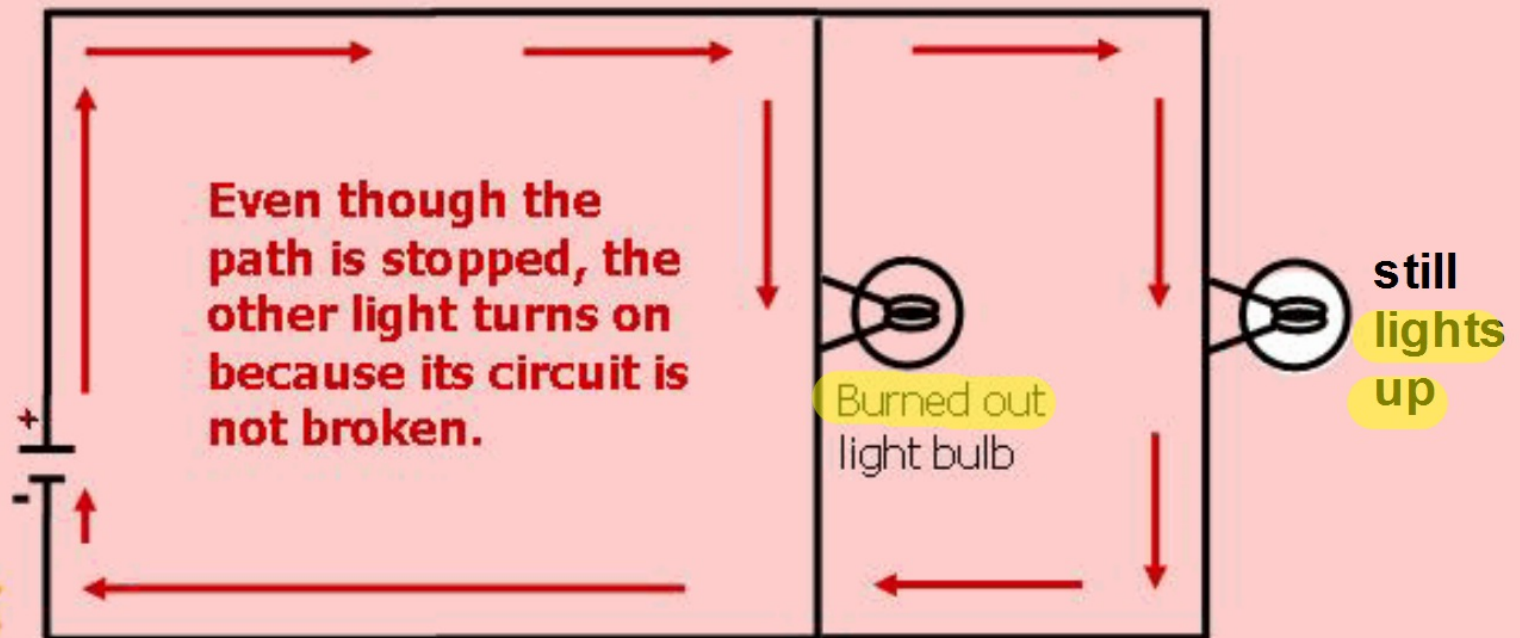**The current divides because it has more than one path to flow.**



**Your house is wired with parallel circuits.**  
**Why do you think this is so?**

# Parallel Circuit Info

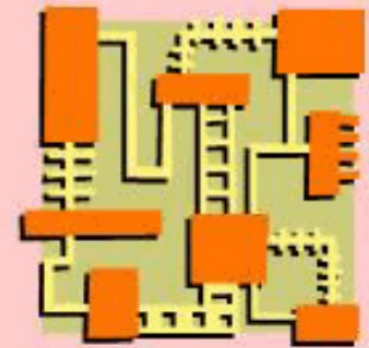

- contains **separate** branches for current to move through
- potential difference (volts) **same** at each branch
- one light off, use other branches to transfer current
- voltage is the **same** across all branch points (think of them as separate series circuits connected to a battery)
- each branch **does NOT** always have the same current, depends on how much **resistance** is in each branch, (desk lamp, power saw)


# Kirchoff's Current Law

- If current flows into a branching point, the **same total current** must flow out again.




**Label the series circuit and the parallel circuit**

P

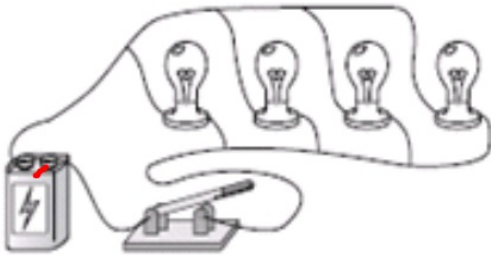


S

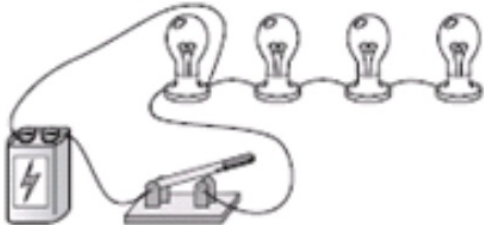

S




S

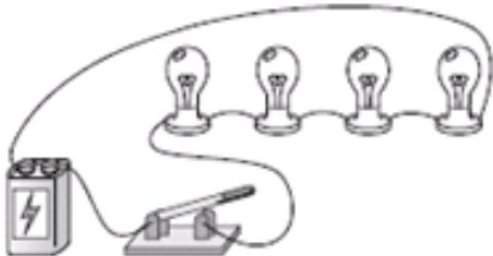


**Which circuit will allow the remaining lights to turn on if one bulb is burnt out?**

Look at the wiring diagrams shown.

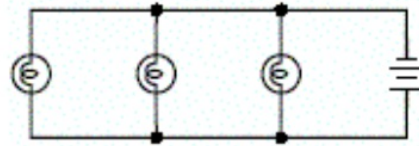


A B C

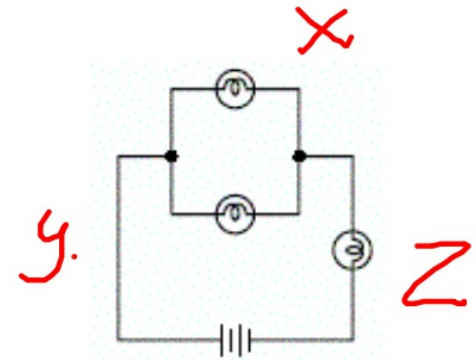

Position and draw a switch in each circuit which would allow you to turn two lights on, and leave one light off.



## Series-parallel

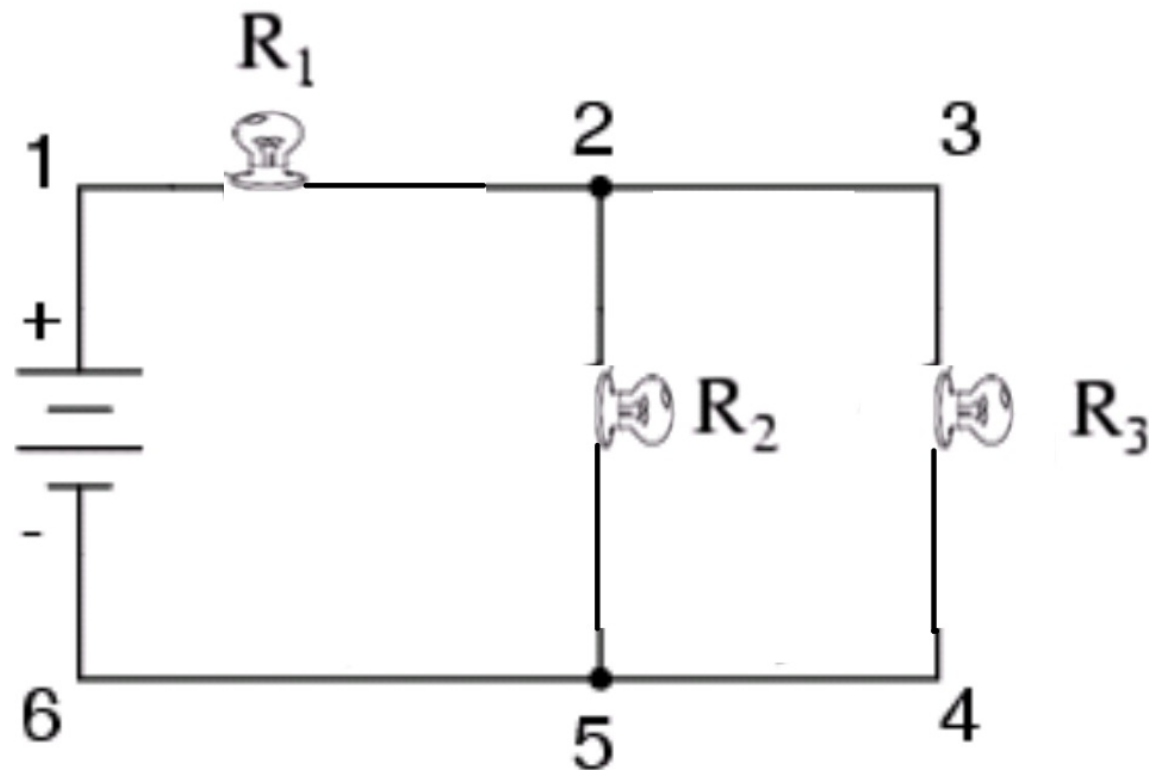

If the bulb at  $R_1$  is burnt out, would the other bulbs stay lit?

**NO**

If the wire was cut at point 4, which bulbs would light (if any)?

**$R_1$  &  $R_2$**


If the bulb at  $R_2$  is missing, would the other two bulbs work?

**YES**

If an open switch was placed at point 3, which bulbs would light?

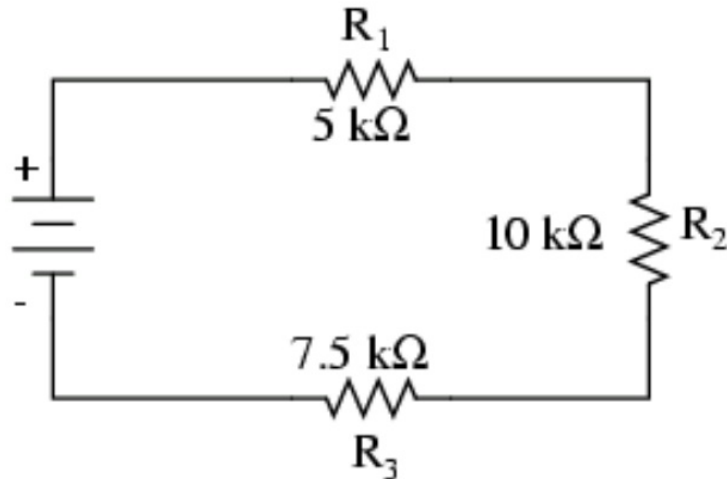**$R_1$  &  $R_2$**

The total resistance in a series circuit is the sum of all the individual resistors.  $R_t = R_1 + R_2 + R_3 \dots$



What is the total resistance in this circuit?

$$R_t = R_1 + R_2 + R_3$$

$$R_t = 5 \text{ k}\Omega + 10 \text{ k}\Omega + 7.5 \text{ k}\Omega$$

$$R_t = 22.5 \text{ k}\Omega$$

If each cell (battery) is 3 V, then what is the total voltage of the circuit? **Two Batteries from the diagram above (Big Line/Little Line Combo)**

$$V = 6 \text{ v}$$

What is the current in the above circuit?

g)  $V = 6 \text{ v}$   
 $R = 22.5 \text{ k}\Omega$

e)  $V = I \cdot R$

s)  $\frac{V}{R} = \frac{I \cdot R}{R}$

s)  $I = \frac{6 \text{ v}}{22.5 \text{ k}\Omega}$

u)  $I = ?$

$$I = \frac{V}{R}$$

$$I = 0.2667 \text{ A}$$